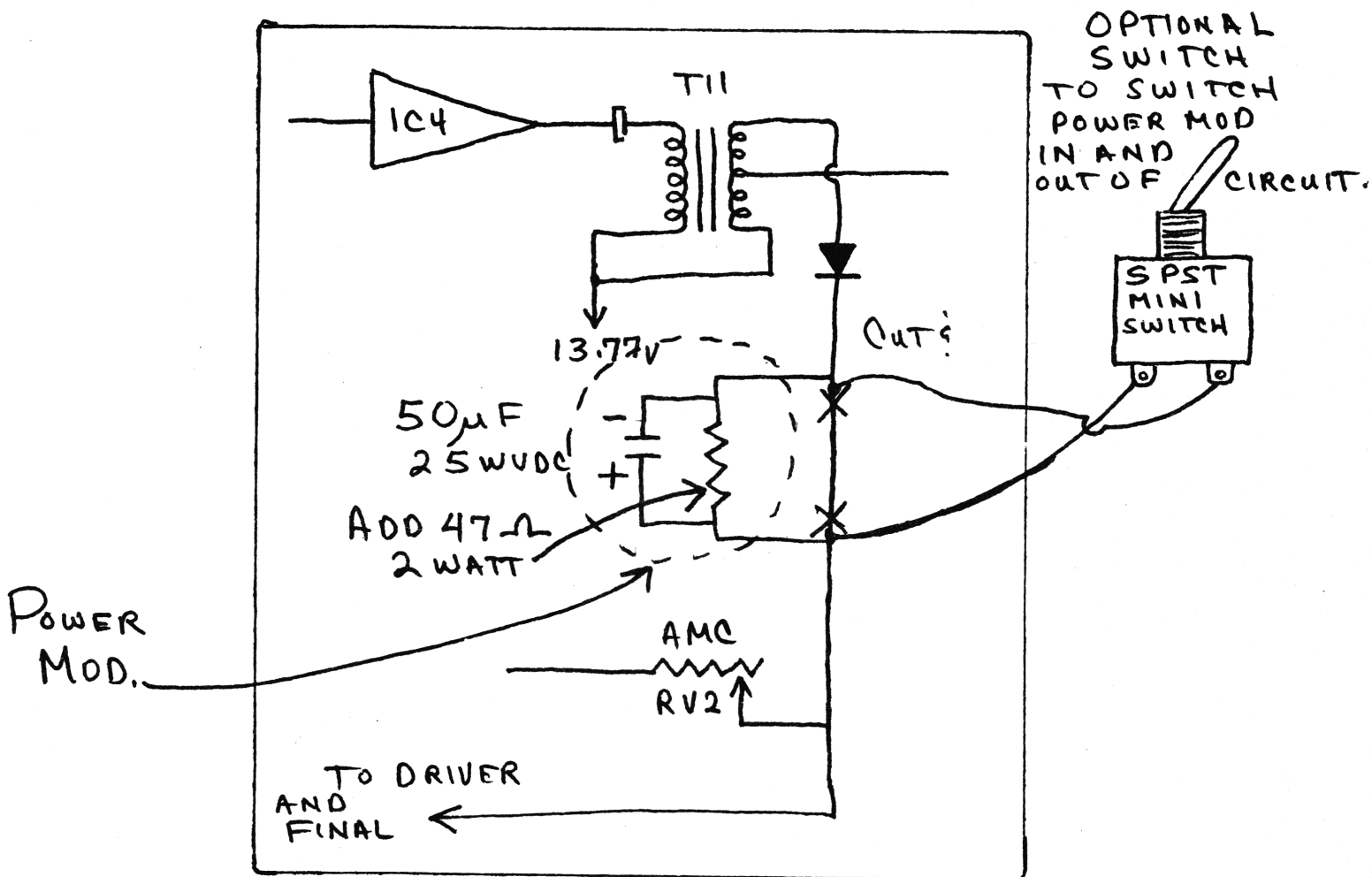


BOMAN BASE CBH-990

SUPER POWER MODULATION MODIFICATION

THEORY:

This modification causes the radio to idle at approximately $\frac{1}{2}$ watt with the mike keyed and modulate to full power when mike is spoken into. This results in very loud audio when heard on the other end. Power Mod circuit may be applied to other circuits. This helpful hint courtesy of my good friend, R. Boyer.



NOTE: THIS MOD. WORKS IN AM MODE ONLY.