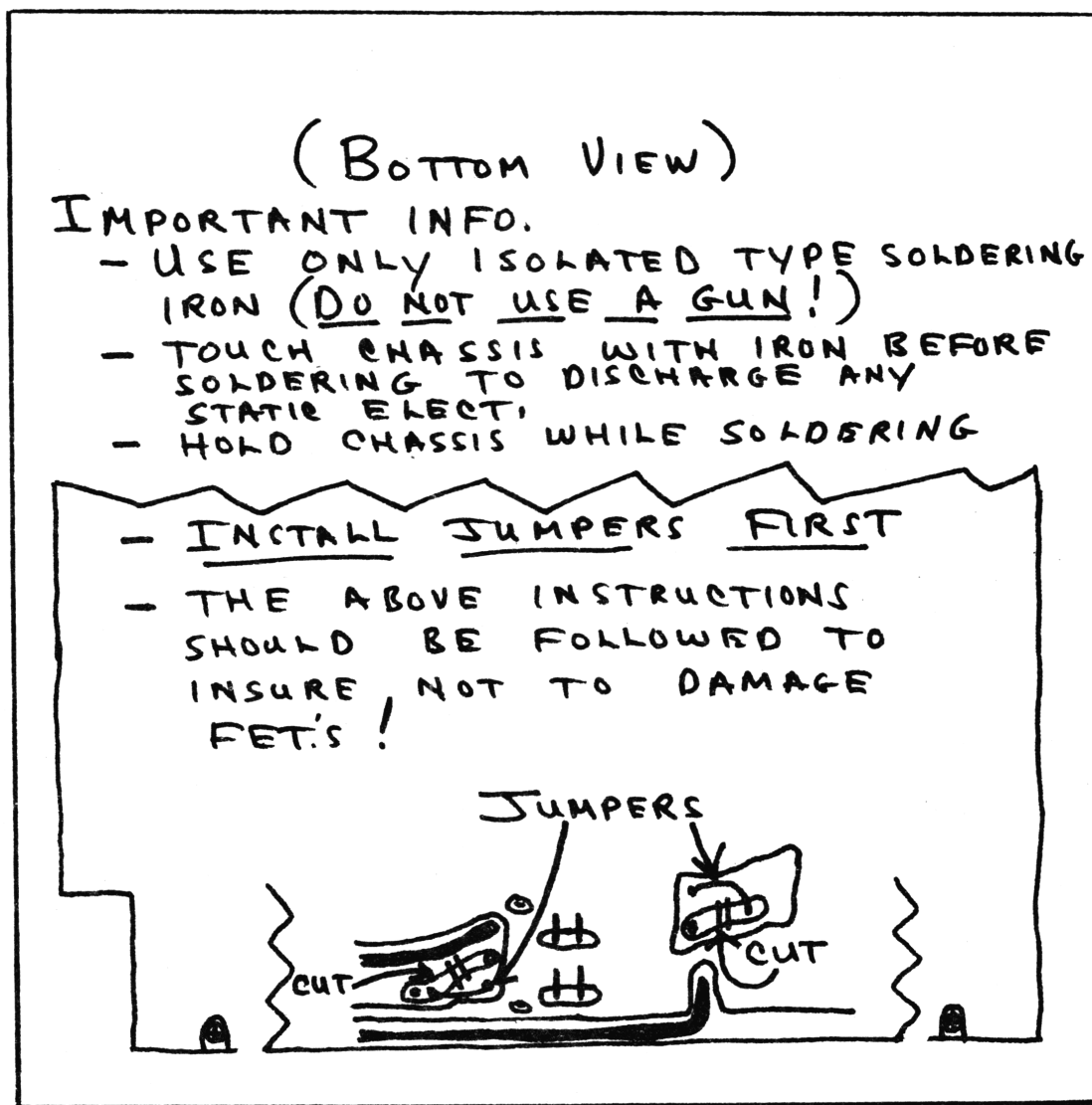


THE "ART OF WIDEBANDING"

AS APPLIED TO 858 UNIDEN CHASSIS
CURES PROBLEM OF POWER DROP
FROM 26 to 28 MHZ



INSTRUCTIONS

1. Locate L-37.
2. Looking at bottom of circuit board, locate areas to be modified (should be near bottom of L37). Cut traces first.
3. Make two cuts as shown by "11". Make two jumpers and place in location as shown.
4. Retune rear slug on "hi freqs.", and front slug on Ch. 1 or "low freq.".