

## BUILD THIS AUDIO TEST STATION

At the present time, resistors R1, R2, R3, & R4 can be purchased from Ramsey Electronics 4/\$1. They are 4 ohm, 10 Watt each. You could also add a scope output in addition to the dummy loads shown below. Or even an audio wattmeter.

