

MB8719 with 11.1125 Crystal

Another diagram layout with: 41-44, & 10KC Flip-Flop....

Frequencies per selector chart was not sent in,

All connections are made directly to the PLL pins indicated, unless marked different.

