

VOLTAGE REGULATOR DESIGN - USING ZENER DIODE

The essential components in a zener voltage regulator are a limiting resistor and the zener.

The zener attempts to maintain a constant voltage (E_z) across itself by drawing the proper amount of current. Several important specifications are necessary in order to acquire the proper diode.


1. Choose the voltage of zener (E_z) you require: Values range from 2.4 to 200 Volts, and current ranges from $\frac{1}{2}$ to 50 Watts.
2. Figure the power rating: $P_z = E_z (I_{load}) (1.25)$. The 1.25 is a safety factor.
3. Figure maximum zener current ($I_z \text{ max.}$): $I_z \text{ max.} = P_z / E_z (.9)$. The 0.9 is the safety factor.
4. Series current limiting resistor is figured by: $R = E_R / I_z \text{ max.}$
 E_R is the voltage drop across the resistor or Voltage input-zener voltage.
5. Power rating of resistor is: $PR = E_R / I_z \text{ max.}$

(R = Resistance; I = Current; E = Voltage; P = Power)

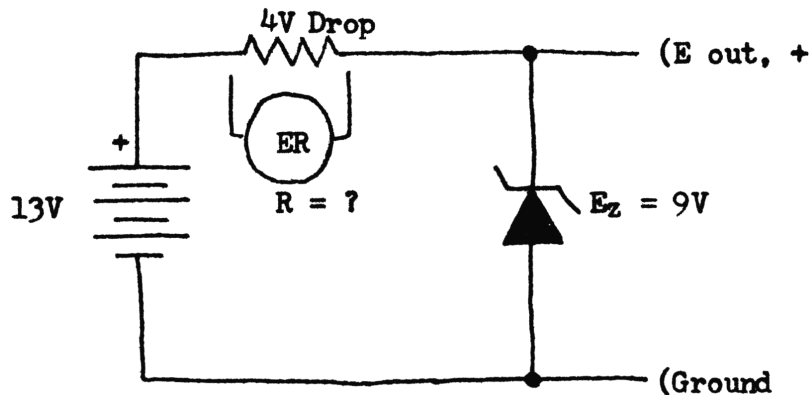Example of circuit requiring a voltage of 9V at 400ma (.4A) is given below:

SPECIFICATIONS

$E_{in} = 13 \text{ Volts}$
 $E_{out} = 9 \text{ Volts}$
 $I_{load \text{ max}} = 400\text{ma} (.4\text{A})$



The following steps are necessary to determine the required circuit value.

1. Since 9V is required output voltage, a 9V zener is used.
 2. Power rating = E_z times I_{load} times (1.25): 9V times .4Amp times 1.25 equals 4.5 Watts. A 5W zener is used as closest value above 4.5 watts.
 3. $I_z \text{ max} = P_z$ divided by E_z times .9: 4.5W divided by 9V times 0.9 equals .45 Amps.
 4. $R = E_R$ divided by I_z : 4V divided by .45 equals 8.88 ohms. A 9.1 ohm resistor is used as closest standard value.
 5. $PR = E_R$ time $I_z \text{ max.}$: 4V times .45 Amps equals 1.8W. So use a 2W resistor. (Note: to be on the safe side always overrate your parts!)
- REMEMBER MURPHY....

So, from the above calculations the specifications of circuit are:
5W, 9V Zener Diode and 2W, 9.1 ohm resistor.....