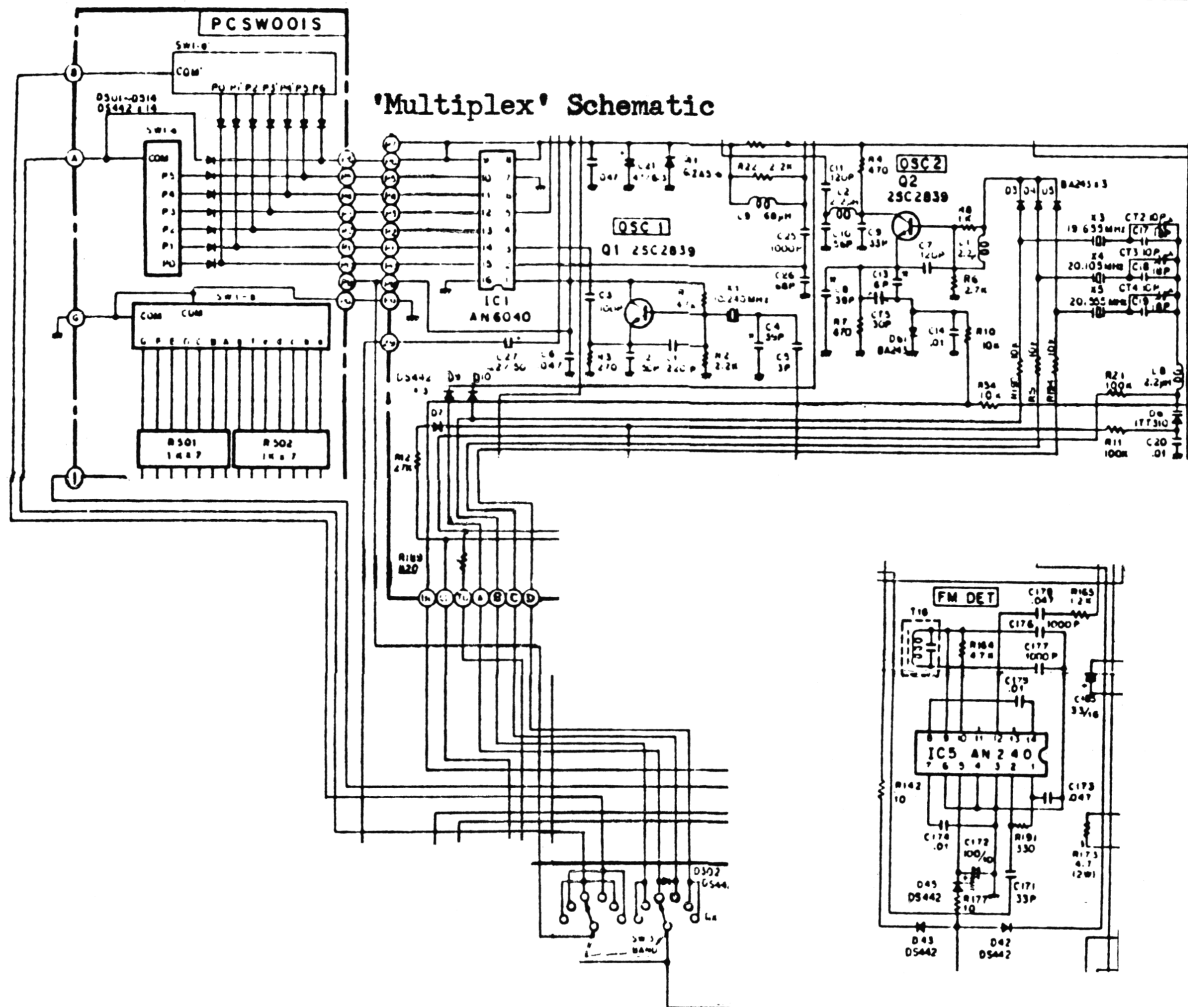


02A 'EXPORT' Chassis: "Multiplex and Direct" Band Switching

"Multiplex" chassis: Will have a varied amount of crystals in OSC 2 circuit, a double rotary band switch, and diode matrix in most cases. The FM DET circuit will have only 1 coil.

"Direct" chassis: Will have a separate crystal for every frequency band in OSC 2 circuit. FM DET circuit will have 2 coils.

Below are "Chopped up" partial schematics, but connections are correct.....



TAKE YOUR CHOICE - WHICH OF THESE WOULD YOU LIKE TO TROUBLESHOOT.....?

'Direct' Schematic

