

NOISE REDUCTION TECHNIQUES FOR SUPER DXING

by J.S.

MOBILE

Parts Required:

- Auto stereo Graphic Equalizer/Power Booster
- Pair of good quality Car Stereo Speakers (prefer 3-way)
- DPDT Switch
- 14 ga. stereo hookup wire

Connect EQ/BOOSTER to CB as shown below. Setup EQ curve to resemble Fig. B., and then experiment to find loudest voice/lowest noise. "WALKMAN" stereo headphones work great tool!


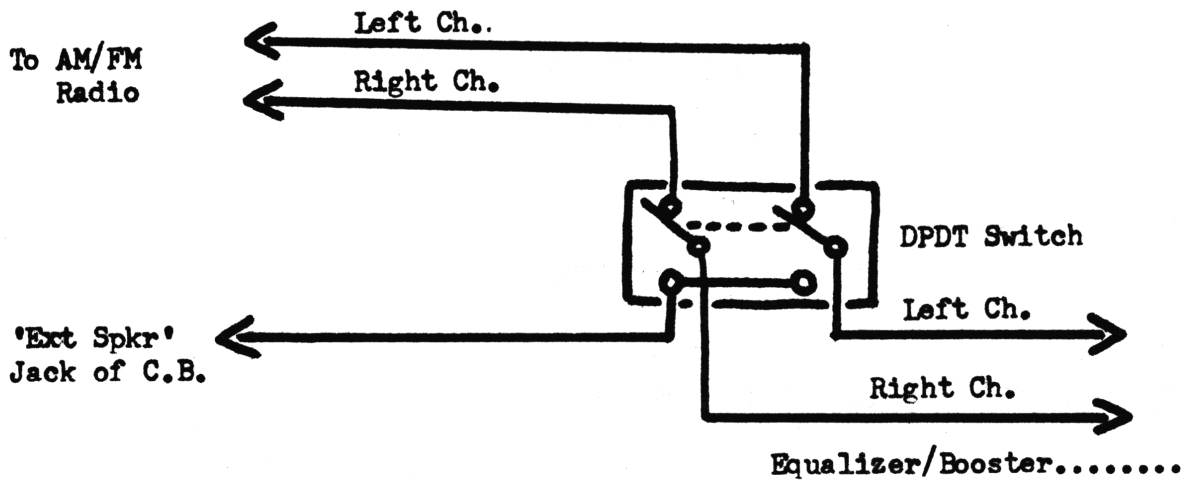


Figure B.

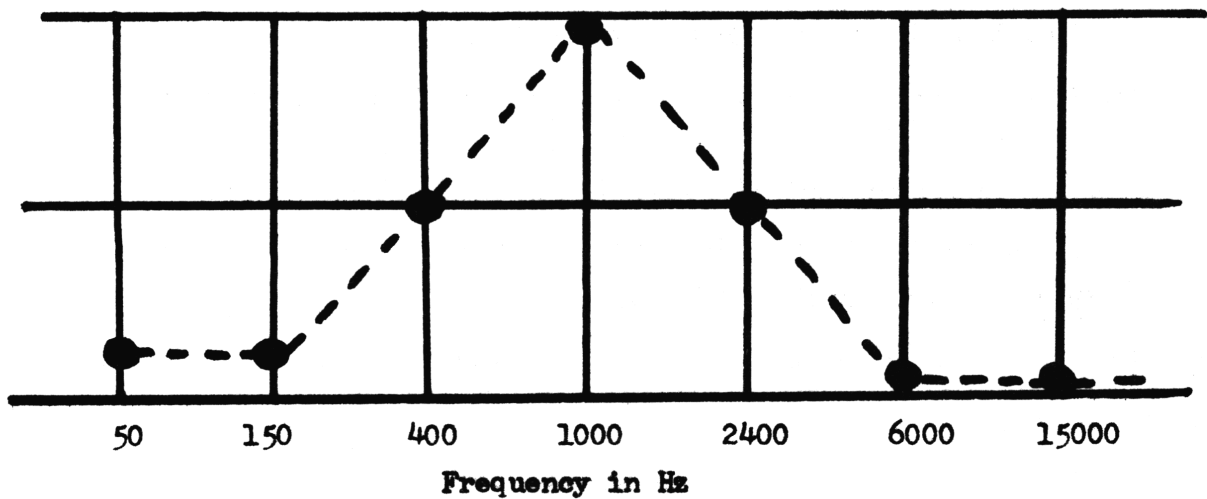

Speech Filter Curve for Equalizer/Booster....