

VARIABLE AM/FM POWER FOR THE HR2510

the voltage back to the R. F. gain control.

(4) Next connect a 4" piece of hookup wire to where the orange wire, in step 2, was removed.

(5) Connect the other end of the hookup wire to R-75, closest to IC 105. This removes the TX frequency adjustment from the circuit

(6) To center the Rit Control, check at pin 16 of IC 301. Adjust L-315 for 10.2400mhz exactly, if needed.

Figure # 2 is a Front View. Connect Orange wire to R-801 side of cut run.


NOTE: Be sure to CAREFULLY cut the circuit on the Back side!

I think this will work on the Lincoln also.

VARIABLE AM/FM POWER FOR THE HR2510

• MARK WASSERMAN

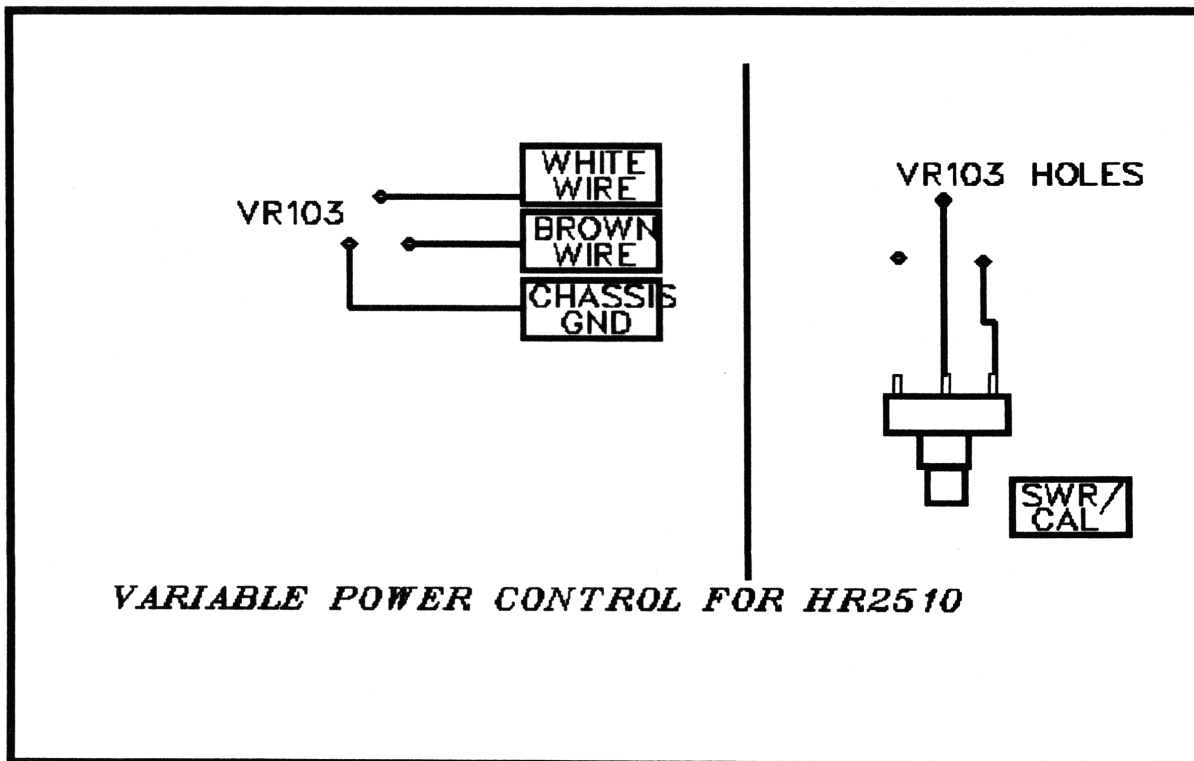NOTE:FOR THE EXPERIENCED TECHNICIAN ONLY.



FIGURE#3..... VARIABLE POWER